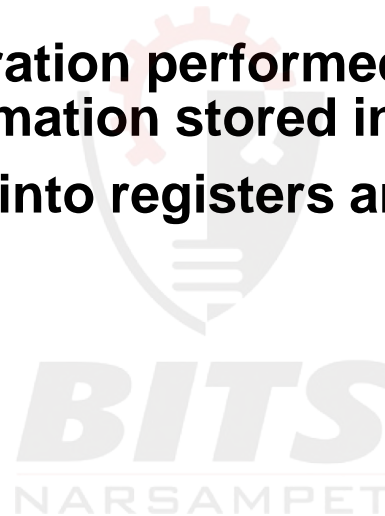


MICROOPERATIONS (1)

- The operations on the data in registers are called microoperations.
- An elementary operation performed (during one clock pulse), on the information stored in one or more registers.
- The functions built into registers are examples of microoperations
 - Shift
 - Load
 - Clear
 - Increment
 - ...



REGISTER TRANSFER LANGUAGE

- Viewing a computer, or any digital system, in this way is called the register transfer level
- This is because we're focusing on
 - The system's registers
 - The data transformations in them, and
 - The data transfers between them.

Rather than specifying a digital system in words, a specific notation is used, *register transfer language*

For any function of the computer, the register transfer language can be used to describe the (sequence of) microoperations

- Register transfer language
 - A symbolic language
 - A convenient tool for describing the internal organization of digital computers
 - Can also be used to facilitate the design process of digital systems.

REGISTER TRANSFER

- Copying the contents of one register to another is a register transfer
- A register transfer is indicated as
- **$R2 \leftarrow R1$**
 - In this case the contents of register R2 are copied (loaded) into register R1
 - A simultaneous transfer of all bits from the source R1 to the destination register R2, during one clock pulse
 - Note that this is a non-destructive; i.e. the contents of R1 are not altered by copying (loading) them to R2
- A register transfer such as

$R3 \leftarrow R5$

Implies that the digital system has

- the data lines from the source register (R5) to the destination register (R3)
- Parallel load in the destination register (R3)
- Control lines to perform the action



BASIC SYMBOLS FOR REGISTER TRANSFERS

Symbols	Description	Examples
Capital letters & numerals	Denotes a register	MAR, R2
Parentheses ()	Denotes a part of a register	R2(0-7), R2(L)
Arrow \leftarrow	Denotes transfer of information	R2 \leftarrow R1
Colon :	Denotes termination of control function	P:
Comma ,	Separates two micro-operations	A \leftarrow B, B \leftarrow A


BUS AND BUS TRANSFER

Bus is a path(of a group of wires) over which information is transferred, from any of several sources to any of several destinations.

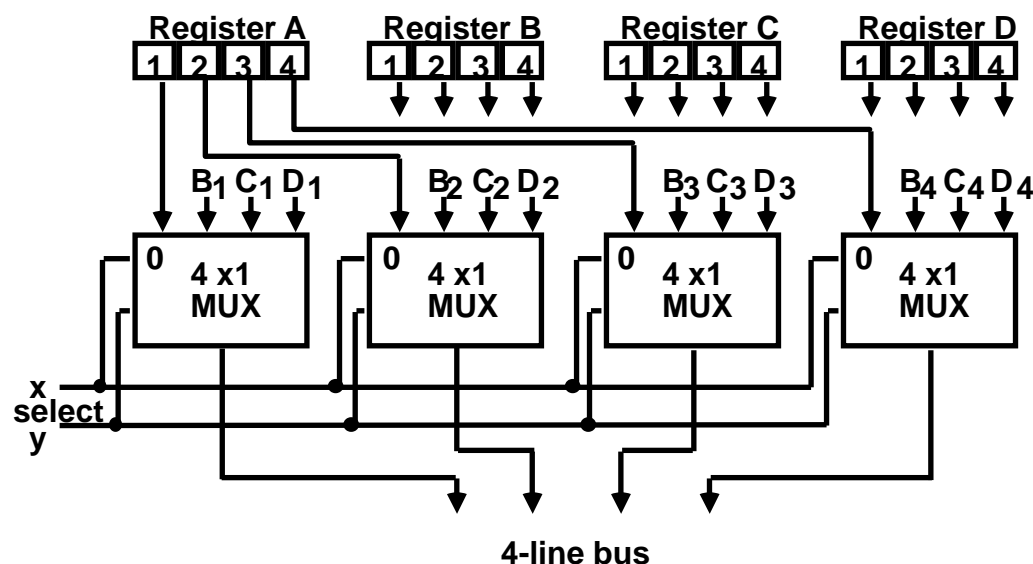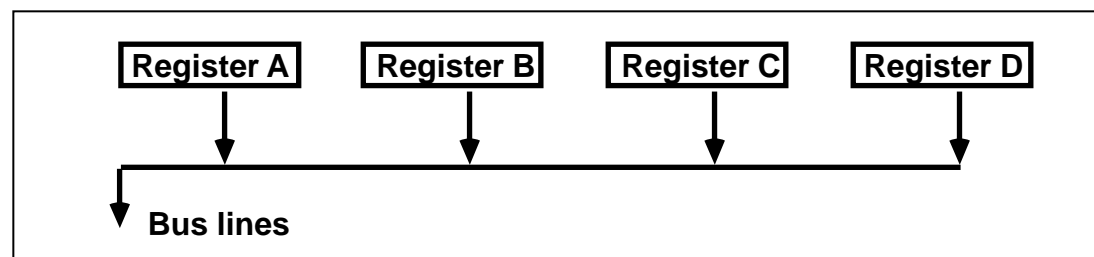From a register to bus: $\text{BUS} \leftarrow R$



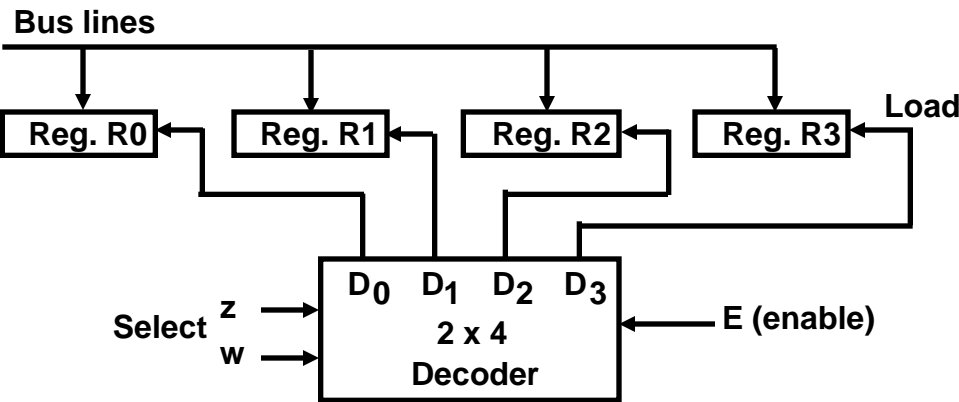TRANSFER FROM BUS TO A DESTINATION REGISTER




Three-State Bus Buffers

Normal input A
Control input C



Bus line with three-state buffers

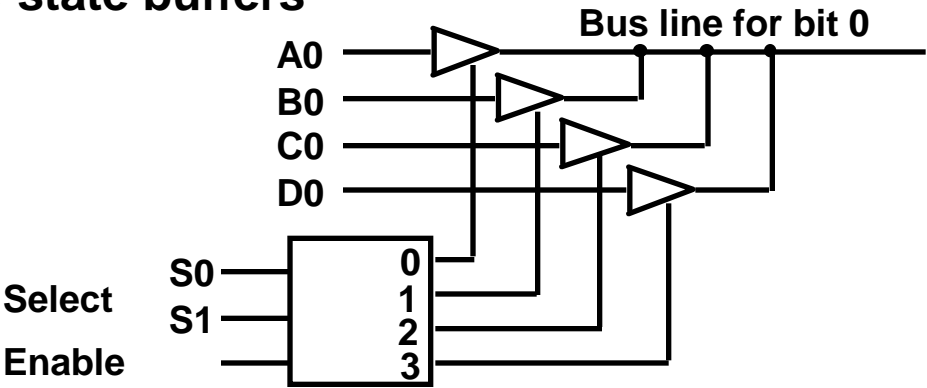

BUS TRANSFER IN RTL

- Depending on whether the bus is to be mentioned explicitly or not, register transfer can be indicated as either

$R2 \leftarrow R1$


or

$BUS \leftarrow R1, R2 \leftarrow BUS$

- In the former case the bus is implicit, but in the latter, it is explicitly indicated


MEMORY (RAM)

- Memory (RAM) can be thought as a sequential circuits containing some number of registers
- These registers hold the *words* of memory
- Each of the r registers is indicated by an *address*
- These addresses range from 0 to $r-1$
- Each register (word) can hold n bits of data
- Assume the RAM contains $r = 2^k$ words. It needs the following
 - n data input lines
 - n data output lines
 - k address lines
 - A Read control line
 - A Write control line

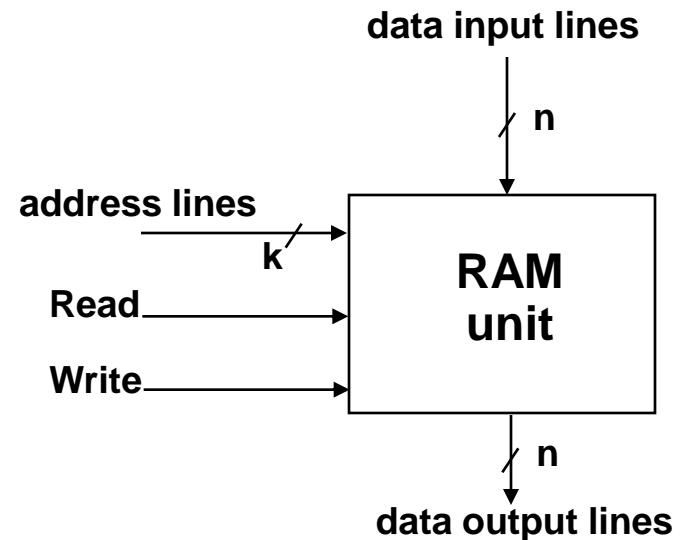

MEMORY TRANSFER

- Collectively, the memory is viewed at the register level as a device, M.
- Since it contains multiple locations, we must specify which address in memory we will be using
- This is done by indexing memory references
- Memory is usually accessed in computer systems by putting the desired address in a special register, the *Memory Address Register (MAR, or AR)*
- When memory is accessed, the contents of the MAR get sent to the memory unit's address lines

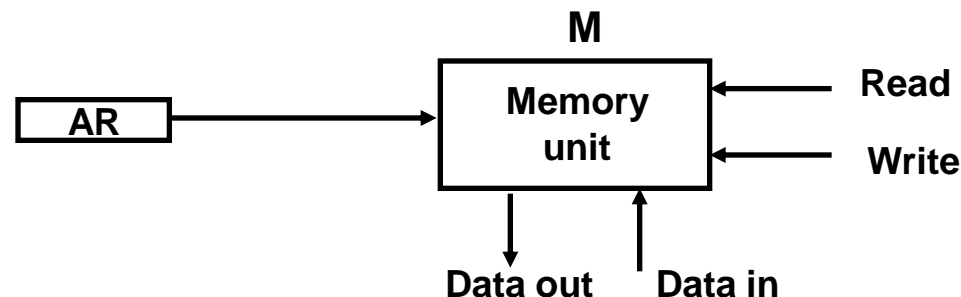

MEMORY READ

- To read a value from a location in memory and load it into a register, the register transfer language notation looks like this:

$R1 \leftarrow M[MAR]$

- This causes the following to occur
 - The contents of the MAR get sent to the memory address lines
 - A Read (= 1) gets sent to the memory unit
 - The contents of the specified address are put on the memory's output data lines
 - These get sent over the bus to be loaded into register R1

MEMORY WRITE

- To write a value from a register to a location in memory looks like this in register transfer language:

$$M[MAR] \leftarrow R1$$

- This causes the following to occur
 - The contents of the MAR get sent to the memory address lines
 - A Write (= 1) gets sent to the memory unit
 - The values in register R1 get sent over the bus to the data input lines of the memory
 - The values get loaded into the specified address in the memory

SUMMARY OF R. TRANSFER MICROOPERATIONS

$A \leftarrow B$

Transfer content of reg. B into reg. A

$AR \leftarrow DR(AD)$

Transfer content of AD portion of reg. DR into reg. AR

$A \leftarrow \text{constant}$

Transfer a binary constant into reg. A

$ABUS \leftarrow R1,$

**Transfer content of R1 into bus A and, at the same time,
transfer content of bus A into R2**

$R2 \leftarrow ABUS$

AR

Address register

DR

Data register

$M[R]$

Memory word specified by reg. R

M

Equivalent to $M[AR]$

$DR \leftarrow M$

**Memory *read* operation: transfers content of
memory word specified by AR into DR**

$M \leftarrow DR$

**Memory *write* operation: transfers content of
DR into memory word specified by AR**

MICROOPERATIONS

- **Computer system microoperations are of four types:**
 - **Register transfer microoperations**
 - **Arithmetic microoperations**
 - **Logic microoperations**
 - **Shift microoperations**

ARITHMETIC MICROOPERATIONS


- The basic arithmetic microoperations are
 - Addition
 - Subtraction
 - Increment
 - Decrement
- The additional arithmetic microoperations are
 - Add with carry
 - Subtract with borrow
 - Transfer/Load
 - etc. ...

Summary of Typical Arithmetic Micro-Operations


$R3 \leftarrow R1 + R2$	Contents of R1 plus R2 transferred to R3
$R3 \leftarrow R1 - R2$	Contents of R1 minus R2 transferred to R3
$R2 \leftarrow R2'$	Complement the contents of R2
$R2 \leftarrow R2' + 1$	2's complement the contents of R2 (negate)
$R3 \leftarrow R1 + R2' + 1$	subtraction
$R1 \leftarrow R1 + 1$	Increment
$R1 \leftarrow R1 - 1$	Decrement

BINARY ADDER / SUBTRACTOR / INCREMENTER


Binary Adder

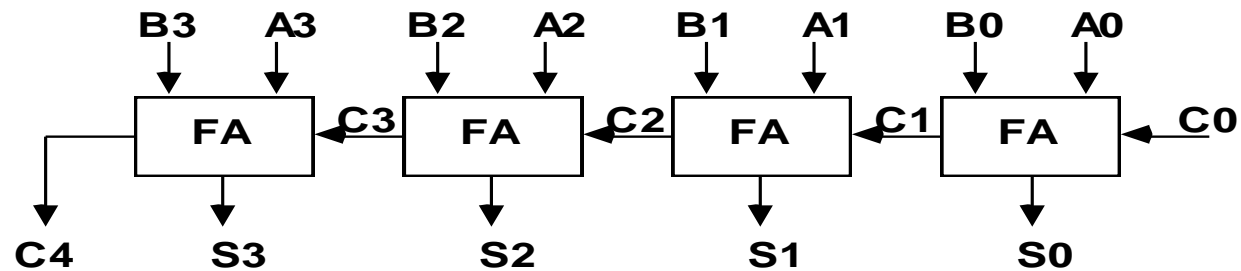


Binary Adder-Subtractor

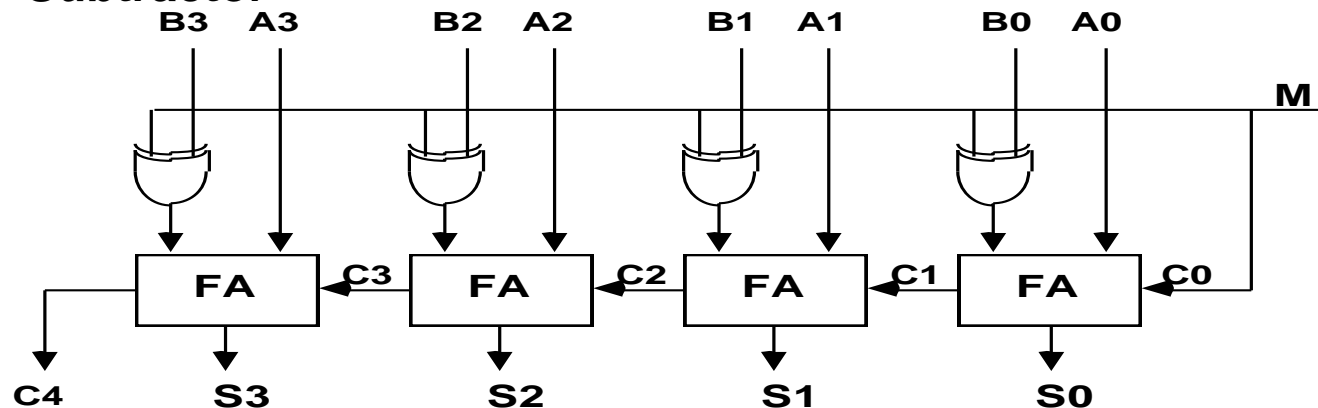

Binary Incrementer

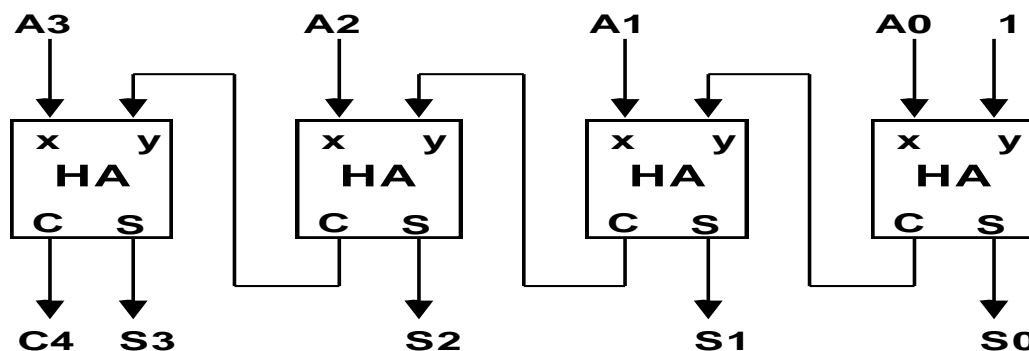

ARITHMETIC CIRCUIT

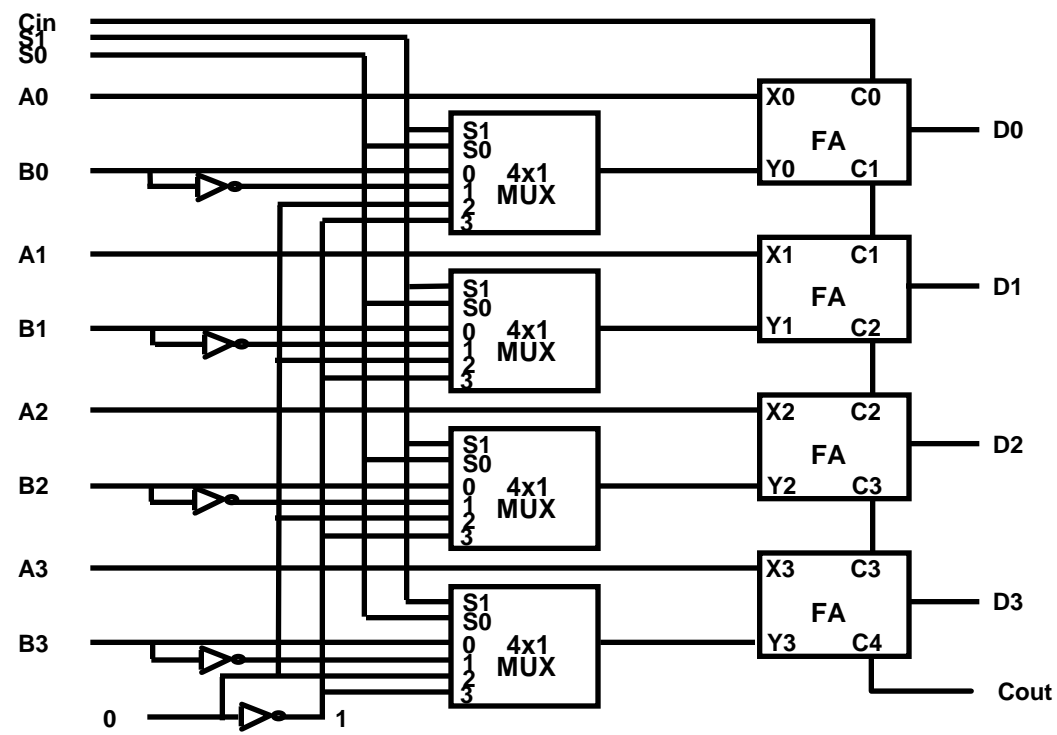

S1	S0	Cin	Y	Output	Microoperation
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	B'	$D = A + B'$	Subtract with borrow
0	1	1	B'	$D = A + B' + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

LOGIC MICROOPERATIONS

- **Specify binary operations on the strings of bits in registers**
 - Logic microoperations are bit-wise operations, i.e., they work on the individual bits of data
 - useful for bit manipulations on binary data
 - useful for making logical decisions based on the bit value
- **There are, in principle, 16 different logic functions that can be defined over two binary input variables**

A	B	F_0	F_1	$F_2 \dots F_{13}$	F_{14}	F_{15}
0	0	0	0	0 ... 1	1	1
0	1	0	0	0 ... 1	1	1
1	0	0	0	1 ... 0	1	1
1	1	0	1	0 ... 1	0	1


- **However, most systems only implement four of these**
 - AND (\wedge), OR (\vee), XOR (\oplus), Complement/NOT
- **The others can be created from combination of these**

LIST OF LOGIC MICROOPERATIONS

- **List of Logic Microoperations**
 - 16 different logic operations with 2 binary vars.
 - n binary vars $\rightarrow 2^{2^n}$ functions
- **Truth tables for 16 functions of 2 variables and the corresponding 16 logic micro-operations**

x	0 0 1 1	<i>Boolean Function</i>	<i>Micro-Operations</i>	<i>Name</i>
y	0 1 0 1			
	0 0 0 0	F0 = 0	F \leftarrow 0	Clear
	0 0 0 1	F1 = xy	F \leftarrow A \wedge B	AND
	0 0 1 0	F2 = xy'	F \leftarrow A \wedge B'	
	0 0 1 1	F3 = x	F \leftarrow A	Transfer A
	0 1 0 0	F4 = x'y	F \leftarrow A' \wedge B	
	0 1 0 1	F5 = y	F \leftarrow B	Transfer B
	0 1 1 0	F6 = x \oplus y	F \leftarrow A \oplus B	Exclusive-OR
	0 1 1 1	F7 = x + y	F \leftarrow A \vee B	OR
	1 0 0 0	F8 = (x + y)'	F \leftarrow (A \vee B)'	NOR
	1 0 0 1	F9 = (x \oplus y)'	F \leftarrow (A \oplus B)'	Exclusive-NOR
	1 0 1 0	F10 = y'	F \leftarrow B'	Complement B
	1 0 1 1	F11 = x + y'	F \leftarrow A \vee B	
	1 1 0 0	F12 = x'	F \leftarrow A'	Complement A
	1 1 0 1	F13 = x' + y	F \leftarrow A' \vee B	
	1 1 1 0	F14 = (xy)'	F \leftarrow (A \wedge B)'	NAND
	1 1 1 1	F15 = 1	F \leftarrow all 1's	Set to all 1's

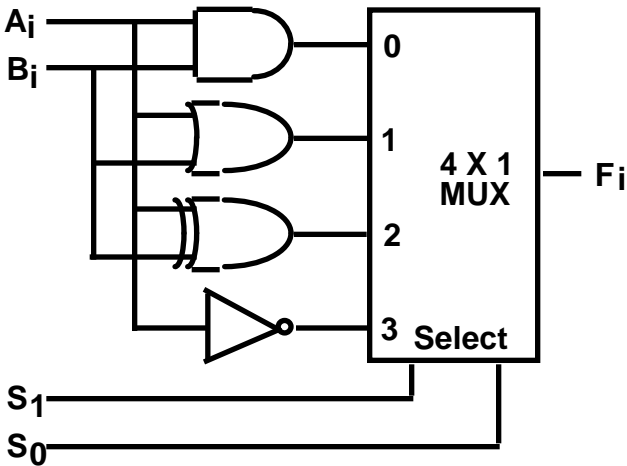HARDWARE IMPLEMENTATION OF LOGIC MICROOPERATIONS



Function table

S_1	S_0	Output	μ -operation
0	0	$F = A \wedge B$	AND
0	1	$F = A \vee B$	OR
1	0	$F = A \oplus B$	XOR
1	1	$F = A'$	Complement

APPLICATIONS OF LOGIC MICROOPERATIONS

- Logic microoperations can be used to manipulate individual bits or a portions of a word in a register
- Consider the data in a register A. In another register, B, is bit data that will be used to modify the contents of A

- | | |
|------------------------|--------------------------------|
| – Selective-set | $A \leftarrow A + B$ |
| – Selective-complement | $A \leftarrow A \oplus B$ |
| – Selective-clear | $A \leftarrow A \cdot B'$ |
| – Mask (Delete) | $A \leftarrow A \cdot B$ |
| – Clear | $A \leftarrow A \oplus B$ |
| – Insert | $A \leftarrow (A \cdot B) + C$ |
| – Compare | $A \leftarrow A \oplus B$ |
| – ... | |

SELECTIVE SET

- In a selective set operation, the bit pattern in B is used to set certain bits in A

1 1 0 0	A_t	
1 0 1 0	B	
<hr/>		
1 1 1 0	A_{t+1}	$(A \leftarrow A + B)$

- If a bit in B is set to 1, that same position in A gets set to 1, otherwise that bit in A keeps its previous value

SELECTIVE COMPLEMENT

- In a selective complement operation, the bit pattern in B is used to *complement* certain bits in A

1 1 0 0	A_t	
1 0 1 0	B	
<hr/>		
0 1 1 0	A_{t+1}	$(A \leftarrow A \oplus B)$

- If a bit in B is set to 1, that same position in A gets complemented from its original value, otherwise it is unchanged

SELECTIVE CLEAR

- In a selective clear operation, the bit pattern in B is used to *clear* certain bits in A

1 1 0 0	A_t	
1 0 1 0	B	
<hr/>		
0 1 0 0	A_{t+1}	$(A \leftarrow A \cdot B')$

- If a bit in B is set to 1, that same position in A gets set to 0, otherwise it is unchanged

MASK OPERATION

- In a mask operation, the bit pattern in B is used to *clear* certain bits in A

1 1 0 0	A_t	
1 0 1 0	B	
<hr/>		
1 0 0 0	A_{t+1}	$(A \leftarrow A \cdot B)$

- If a bit in B is set to 0, that same position in A gets set to 0, otherwise it is unchanged

CLEAR OPERATION

- In a clear operation, if the bits in the same position in A and B are the same, they are cleared in A, otherwise they are set in A

1 1 0 0	A_t	
1 0 1 0	B	
<hr/>		
0 1 1 0	A_{t+1}	$(A \leftarrow A \oplus B)$

INSERT OPERATION


- An insert operation is used to introduce a specific bit pattern into A register, leaving the other bit positions unchanged
- This is done as
 - A mask operation to clear the desired bit positions, followed by
 - An OR operation to introduce the new bits into the desired positions
 - Example
 - » Suppose you wanted to introduce 1010 into the low order four bits of A:

1101 1000 1011 0001	A (Original)
1101 1000 1011 1010	A (Desired)


» 1101 1000 1011 0001	A (Original)
1111 1111 1111 0000	Mask
<hr/>	
1101 1000 1011 0000	A (Intermediate)
0000 0000 0000 1010	Added bits
<hr/>	
1101 1000 1011 1010	A (Desired)

SHIFT MICROOPERATIONS

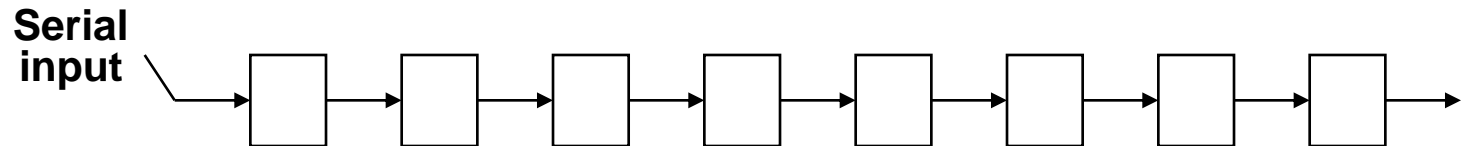- There are three types of shifts
 - *Logical shift*
 - *Circular shift*
 - *Arithmetic shift*
- What differentiates them is the information that goes into the serial input
- A right shift operation




- A left shift operation

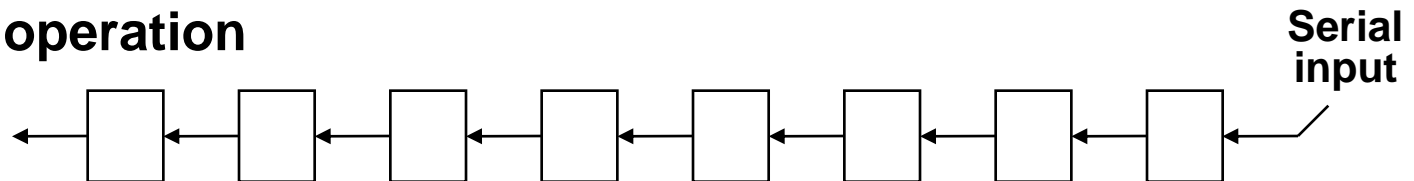


LOGICAL SHIFT

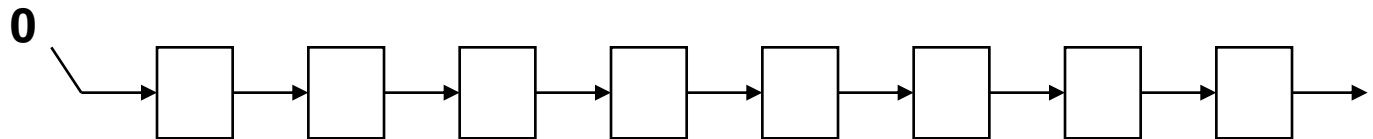- In a logical shift the serial input to the shift is a 0.
- A right logical shift operation:



- A left logical shift operation:

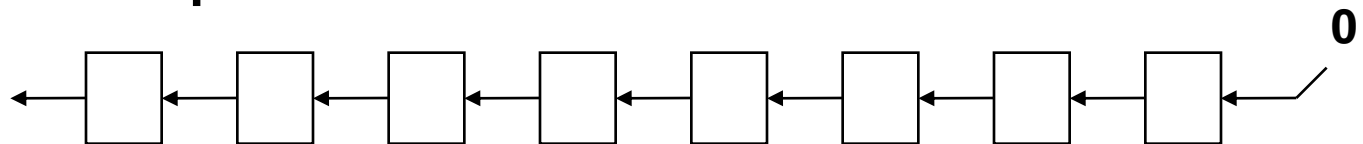


- In a Register Transfer Language, the following notation is used
 - *shl* for a logical shift left
 - *shr* for a logical shift right
 - Examples:
 - » $R2 \leftarrow shr\ R2$
 - » $R3 \leftarrow shl\ R3$


CIRCULAR SHIFT

- In a circular shift the serial input is the bit that is shifted out of the other end of the register.

- A right circular shift operation:

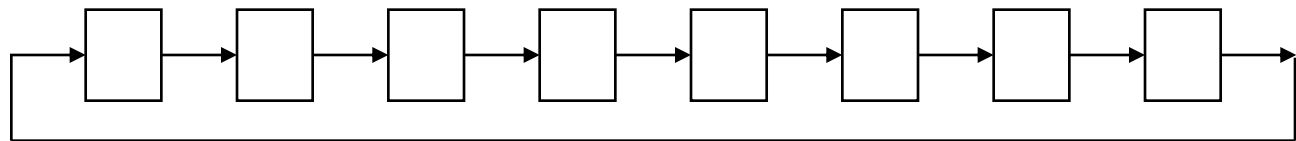


- A left circular shift operation:

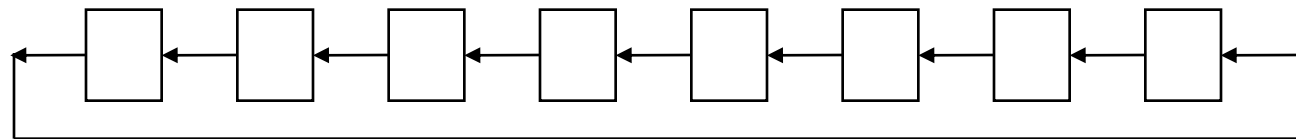


- In a RTL, the following notation is used
 - *cil* for a circular shift left
 - *cir* for a circular shift right
 - Examples:
 - » $R2 \leftarrow cir\ R2$
 - » $R3 \leftarrow cil\ R3$

ARITHMETIC SHIFT

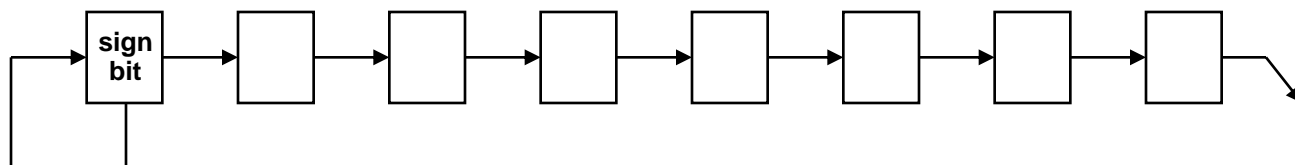- An arithmetic shift is meant for signed binary numbers (integer)
- An arithmetic left shift **multiplies** a signed number **by two**
- An arithmetic right shift **divides** a signed number **by two**
- The main distinction of an arithmetic shift is that it must keep the sign of the number the same as it performs the multiplication or division
- A right arithmetic shift operation:




- A left arithmetic shift operation:

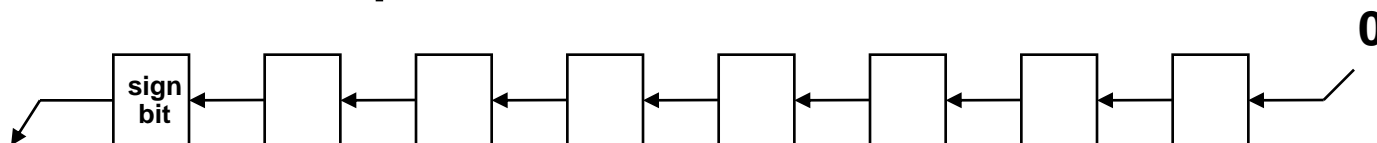


ARITHMETIC SHIFT

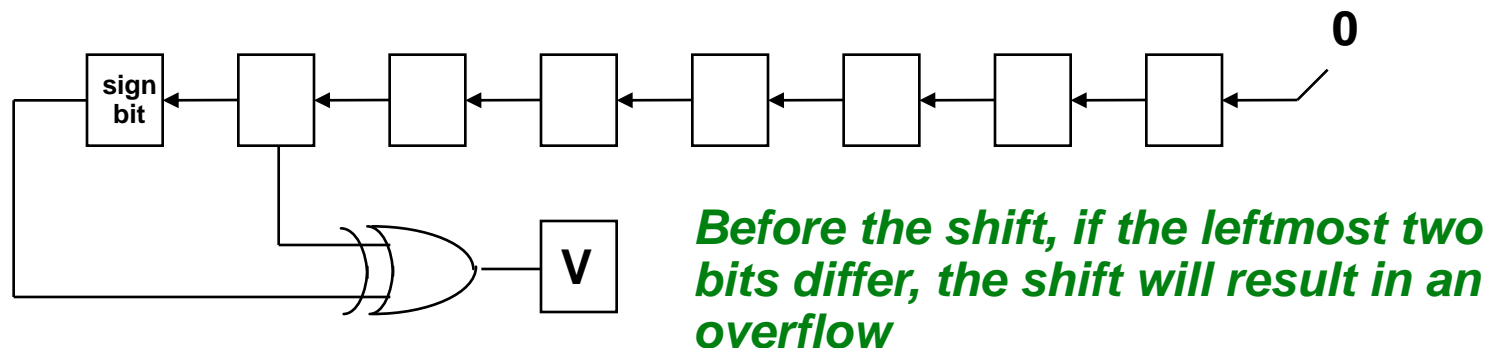- An left arithmetic shift operation must be checked for the **overflow**




- In a RTL, the following notation is used
 - *ashl* for an arithmetic shift left
 - *ashr* for an arithmetic shift right
 - Examples:
 - » $R2 \leftarrow ashr R2$
 - » $R3 \leftarrow ashl R3$

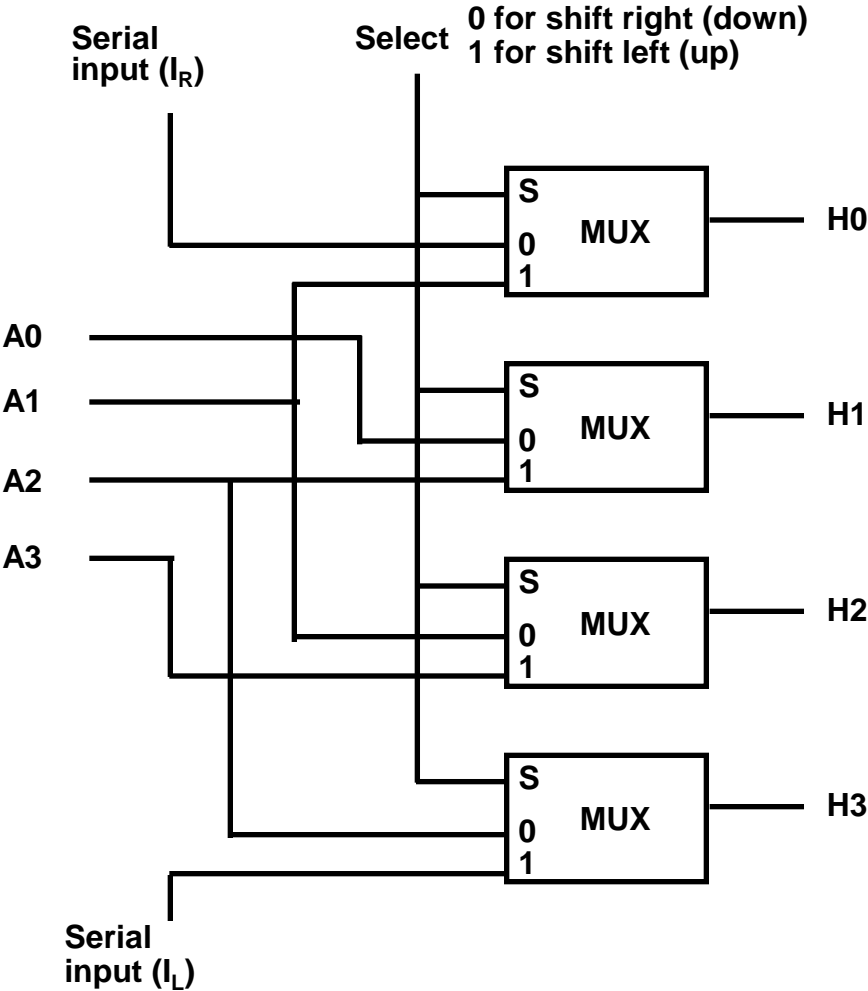HARDWARE IMPLEMENTATION OF SHIFT MICROOPERATIONS



ARITHMETIC LOGIC SHIFT UNIT

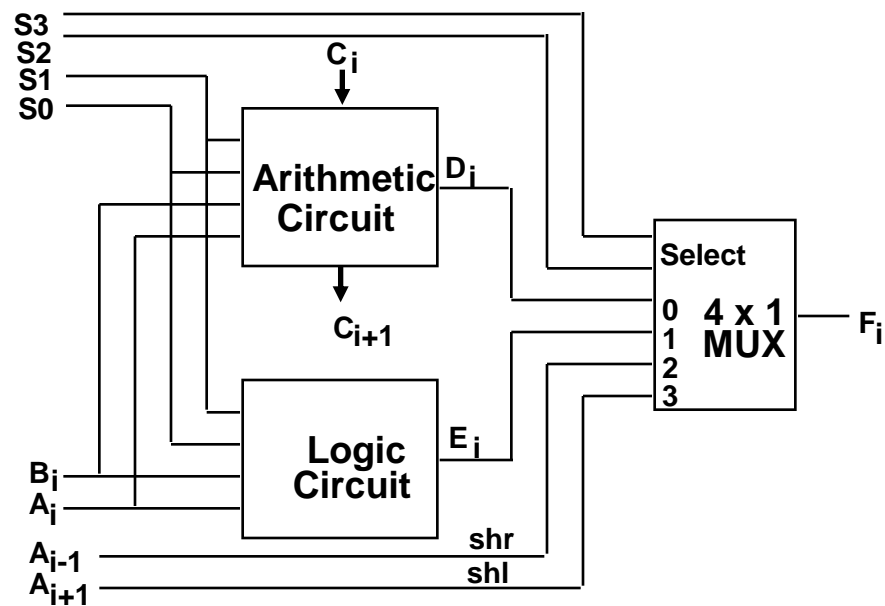

S3	S2	S1	S0	Cin	Operation	Function
0	0	0	0	0	$F = A$	Transfer A
0	0	0	0	1	$F = A + 1$	Increment A
0	0	0	1	0	$F = A + B$	Addition
0	0	0	1	1	$F = A + B + 1$	Add with carry
0	0	1	0	0	$F = A + B'$	Subtract with borrow
0	0	1	0	1	$F = A + B' + 1$	Subtraction
0	0	1	1	0	$F = A - 1$	Decrement A
0	0	1	1	1	$F = A$	Transfer A
0	1	0	0	X	$F = A \wedge B$	AND
0	1	0	1	X	$F = A \vee B$	OR
0	1	1	0	X	$F = A \oplus B$	XOR
0	1	1	1	X	$F = A'$	Complement A
1	0	X	X	X	$F = shr\ A$	Shift right A into F
1	1	X	X	X	$F = shl\ A$	Shift left A into F